

64 kHz $\pm 10V$

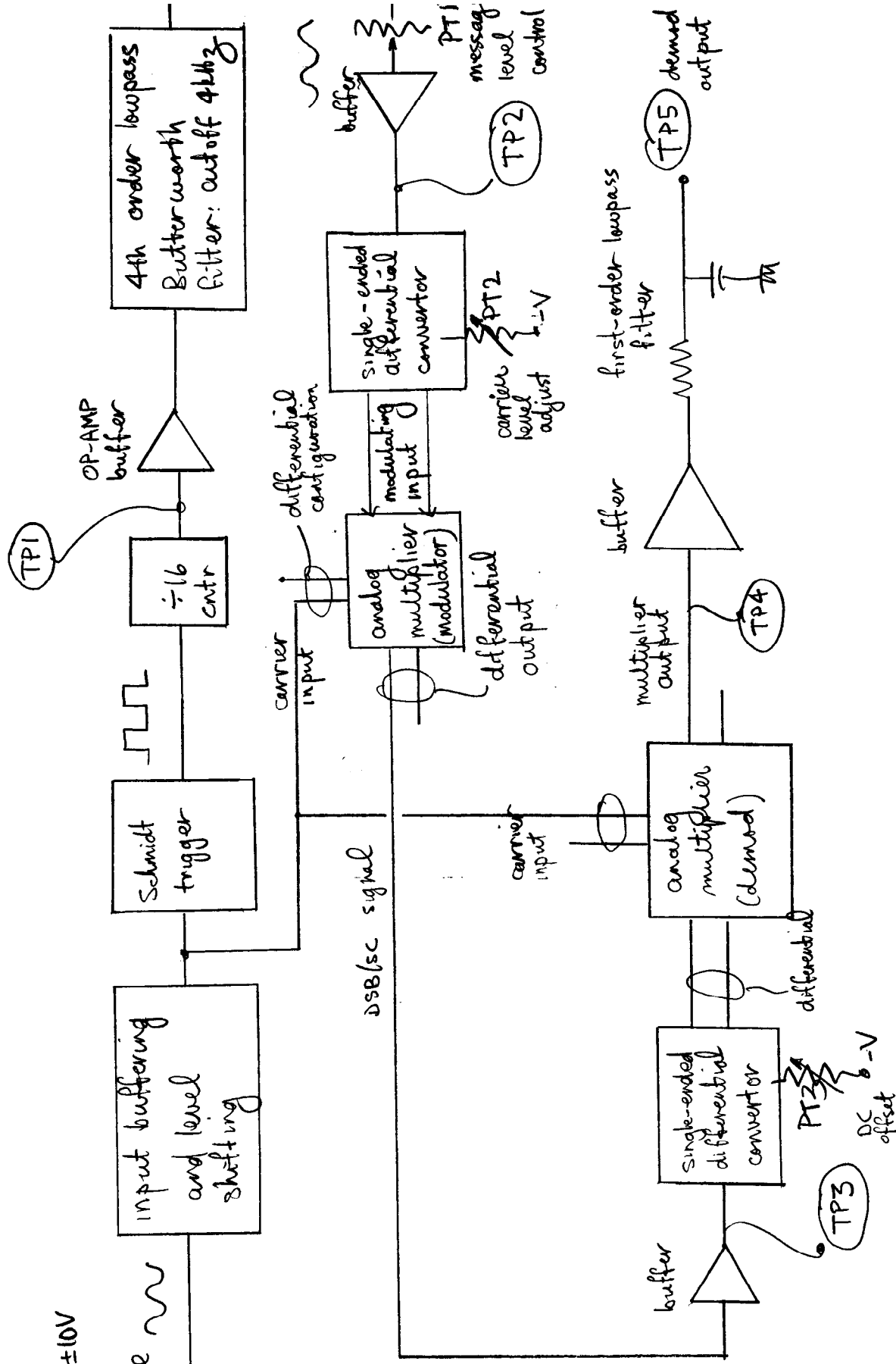


Fig. 1 Block diagram of AM modulator - demodulator circuit

AM Modulator - Demodulator Detailed Schematic

4th-order low-pass Butterworth filter

